

Resistance and Electric Power

Recall:

Voltage, V is the electrical energy per unit charge, $V = \text{energy}/q$ in units of volts, $1 \text{ V} = 1 \text{ J/C}$ (analagous to height and gravitational energy)

Current, I is the amount of charge passing per unit time - direction is positive charge (opposite of electron flow)

$I = q/t$ units Ampère, $A = C/s$

Resistance, R

is the ratio of Voltage across an element to current through the element

$$R = V/I$$

units: Ohms, $\Omega = V/A = \text{Js}/C^2$

Let's look at the voltage across and the current through some circuit elements

Resistor a light bulb and a LED

$VI = \text{J/C} \times C/s = \text{J/s}$ hey that's Watts, W unit for

power, $P=VI$


Element	V(V)	I(A)	$R=V/I$	$P=VI$	description
Resistor	1.7	4.8mA	354 Ω	8.2mW	not much
	1.9	5.2mA	365 Ω	9.9mW	ditto

For an Ohmic device, the resistance is constant over a range of Voltages and currents.



For a non-ohmic device, the resistance changes.

diodes

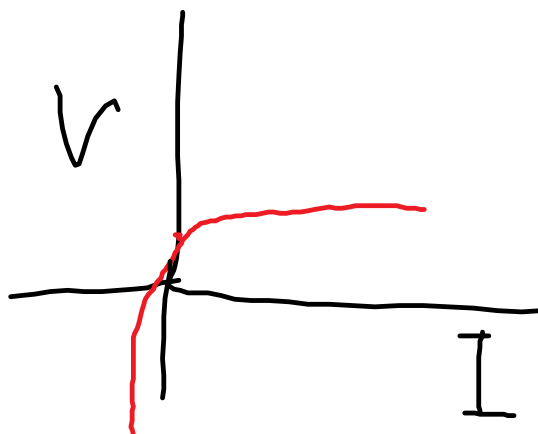

the resistance is still the ratio of V/I at that point and the power output is still VI at that point.

Resistors assume to be Ohmic
what's the point of resistors?

- They dissipate electrical energy as heat, so they
1. can be used to heat stuff like a stove/oven
 2. can protect sensitive elements that smoke and fry with too much heat.
 3. tune frequencies in LCR circuits (old radios)
 4. control the voltage - variable resistors are called rheostats or potentiometers - control potential.

eg.

My kettle is listed at 1.2 kW on a 120V input.

- a) How much energy as heat is produced in 2.0 minutes?
- b) what is the current through the element of the kettle?
- c) what is the resistance of the kettle element?
- d) if only 1.1×10^5 J are transferred to the water, what is the efficiency of the kettle? Where did the excess energy go?

p478 Q21-31 odds

Horsepower, 1 hp = 746W

My kettle is listed at 1.2 kW on a 120V input.

- a) How much energy as heat is produced in 2.0 minutes?

$$\text{energy} = \text{power} \times \text{time} = 1.2 \times 1000 \text{ J/s} \times 2 \times 60\text{s} = 1.4 \times 10^5 \text{ J or } 140 \text{ kJ}$$

$$= 1.4 \times 10^5 \text{ J or } 140 \text{ kJ}$$

b) what is the current through the element of the kettle?

$$P=VI \text{ so } I=P/V = 1200/120=10 \text{ A}$$

c) what is the resistance of the kettle element?

$$R=V/I = 120\text{V}/10\text{A} = 12 \Omega$$

d) if only $1.1 \times 10^5 \text{ J}$ are transferred to the water, what is the efficiency of the kettle? Where did the excess energy go?

efficiency = energy out/ energy in x 100%

$$= 1.1 \times 10^5 \text{ J} / 1.4 \times 10^5 \text{ J} \times 100\% = 79\%$$

mass of water

$$Q = mc\Delta T$$

heat in J

↑

4180 J / K°C for water

↑

Temperature

Recall:

Voltage, V, the energy per unit charge

$V = \text{energy}/q$ in volts $1V = 1J/C$
(like height and gravitational energy)

Current, I , the amount of charge passing per unit time, in Ampères, $1A = 1C/s$


Let's look at the current and voltage properties of a resistor and an LED light.

unit analysis

$VI = VA = J/\cancel{C} \times \cancel{C}/s = J/s = \text{Watt}, W$ the unit of power, so $P = VI$

Element	V(V)	I(mA)	$R = V/I$ (Ω)	$P = VI$ (W)	observe
resistor	5.5	16.1	0.34 k Ω	89mW	not much
resistor	11.6	33.5	0.35 k Ω	389mW	ditto
resistor					
LED	1.9	1.9	1.0 k Ω	3.6mW	bright
LED	1.8	1.0	1.8 k Ω	1.8mW	less bright
LED					

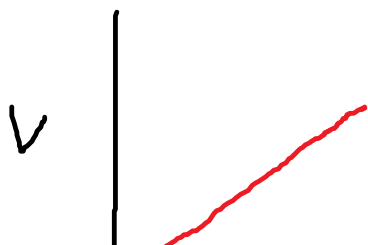Ohmic elements - the resistance, $R = V/I$ in ohms, Ω , is constant over a range of voltages.






slope is constant, $= R$

non-ohmic element - the resistance changes

LED - light emitting diode

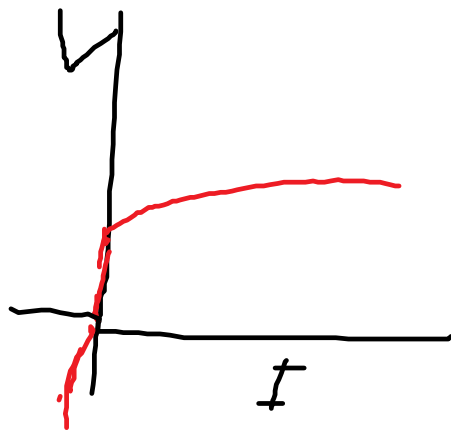

slope is not $= R$, R is just the ratio of V/I for a particular set of V and I .

What is a resistor? What is it for?

it can control the current for a set voltage but usually it is used to transform electrical energy into heat or light.

light bulb - changes electrical energy into light and heat.

electrical stove/oven changes electrical energy into heat.

dissipate heat to protect sensitive circuit elements

variable resistor - called a rheostat or potentiometer - controlling the voltage

eg. my kettle is listed at 1500W for a 120V input.

What is the

- a) current through the heating element?
- b) how much charge goes through the element in 2.0 minutes?
- c) resistance of the heating element?
- d) how much energy is used by the element over 2.0 minutes?
- e) if you measure the heat absorbed by the water as $1.4 \times 10^5 \text{J}$, how much energy is lost? What is the efficiency of the kettle? Where did the lost energy go?

p478 Q21-31 odds (Q1-9 odds)

eg. my kettle is listed at 1500W for a 120V input.

What is the

- a) current through the heating element?

$$P=VI \quad I=P/V = 1500\text{W}/120\text{V} = 12.5\text{A}$$

- a) how much charge goes through the element in 2.0 minutes?

$$q=It = 12.5 \text{ A} \times 120\text{s} = 1500\text{C}$$

- a) resistance of the heating element?

$$R=V/I = 120/12.5=9.6 \Omega$$

$$\text{or } R=V^2/P = 120^2/1500 = 9.6\Omega$$

a) how much energy is used by the element over 2.0 minutes?

$$\text{energy} = Pt = 1500\text{W} \times 120\text{s}$$
$$1500 \times 120 = 180000 = 180\text{kJ}$$

b) if you measure the heat absorbed by the water as $1.4 \times 10^5\text{J}$, how much energy is lost? What is the efficiency of the kettle? Where did the lost energy go?

40 kJ is lost (180-140)

$$\text{efficiency} = 140\text{kJ}/180\text{kJ} \times 100\%$$
$$= 78\%$$

energy is lost to the air through conduction, convection and some radiation.

$$Q = mc\Delta T$$

Q is heat

m is mass

c is specific heat capacity, water = $4180\text{J/kg}^\circ\text{C}$

T is temperature

Resistance and Power

Recall:

What is voltage and current?

Voltage, V, is the energy per unit charge,

$V = \text{energy}/q$ in units of Volts, V $1V=1J/C$

Current, I , is the amount of charge passing per unit time, $I=q/t$, in units of Ampère, A $1A = 1C/s$

What is resistance, R ?

define resistance as the ratio of voltage to current

$R=V/I$ units of Ohms $\Omega= V/A$

If an element has a large resistance, the current will be less for the same voltage.

Let's try to observe the voltage/current properties of a resistor and an LED light.


unit analysis

$V \times I = J/C \times C/s = J/s = W = \text{unit for power}$

$P=VI$

Element	V(V)	I(A)	$R=V/I(\Omega)$	$P=VI(W)$
Resistor 1	0.047	133 μA	350 Ω	6.3 μW
2	0.054	149 μA	360 Ω	8.0 μW
3	0.023	66 μA	350 Ω	1.5 μW
LED	1.7	10 μA	0.17 M Ω	17 μW
	1.8	93 μA	19k Ω	170 μW
	1.0	0 μA	??? infinite?	0 W

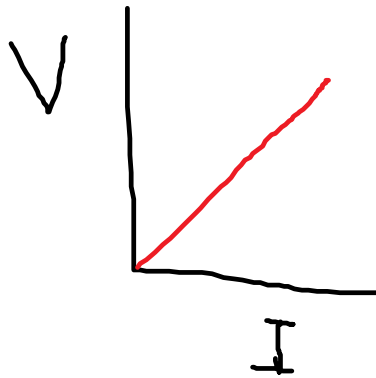Ohmic circuit elements have a constant resistance over a range of voltages - Resistors.



slope is the resistance, $R = V/I$

non- Ohmic circuit elements have a variable resistance. - most lamps and definitely LEDs

LED



slope is not the resistance, $R=V/I$ at each point

eg. My kettle is rated at 1500W when connected to a 120V wall socket. It takes 2.0 minutes to boil 350 g of water, heat capacity 4180 J/kg°C from 15°C to boiling at 100°C.

a) What is the current through the heating element?

$$P=VI \quad I=P/V = 1500/120=12.5 \text{ A}$$

b) How much charge goes through the element in 2.0 minutes?

$$I=q/t \quad \text{so } q = It = 12.5 \times 2 \times 60 = 1,500 \text{ C}$$

c) How much energy is required to heat 350 g of water

from 15 to 100°C ($Q=mc\Delta T$)

$$Q = 0.35 \times (4180) \times (100 - 15) = 124355.0 = 124 \text{ kJ}$$

d) How much energy does the kettle require if it takes 1500W for 2.0 minutes?

$$P = \text{energy/time} \quad \text{energy} = Pt = 1500 \times 2 \times 60 = 180000 = 180 \text{ kJ}$$

e) what is the efficiency of the kettle? Where did the waste energy go?

$$\text{efficiency} = \text{energy out/energy in} \times 100\%$$

$$= 124 \text{ kJ} / 180 \text{ kJ} \times 100 = 124 / 180 = 0.6889$$

69% energy is lost to steam and conduction/convection with the air

f) what is the resistance of the kettle element?

$$120 / 12.5 = 9.6$$

$$R = V/I = V^2/P \quad 120 \times 120 / 1500 = 9.6 \, \Omega$$

p478 Q 21-31 odds